

Standard transfer function for Universal filter

$$\Rightarrow \frac{a_2 s^2 + a_1 s + a_0}{1 + \frac{s}{\omega_0 \cdot Q} + \frac{s^2}{\omega_0^2}}$$

→ By putting value of $a_0, a_1, a_2 \rightarrow$ all four T.F can be achieved.

L.P.F

$$\frac{V_{03}}{V_i} = \frac{+H_0}{1 + \frac{s}{\omega_0 \cdot Q} + \frac{s^2}{\omega_0^2}}$$

$$So, \boxed{a_0 = H_0}, \quad \boxed{a_1 = 0, a_2 = 0}$$

H.P.F

$$\frac{V_{01}}{V_i} = \frac{\frac{H_0}{\omega_0^2} s^2}{1 + \frac{s}{\omega_0 \cdot Q} + \frac{s^2}{\omega_0^2}}$$

$$So, \boxed{a_2 = \frac{H_0}{\omega_0^2}}$$

B.P.R

$$\frac{V_{02}}{V_i} = \frac{-\frac{H_0}{\omega_0} s}{1 + \frac{s}{\omega_0 \cdot Q} + \frac{s^2}{\omega_0^2}}$$

$$So, \boxed{a_1 = -H_0/\omega_0}$$

B.S.F

$$\frac{V_{O4}}{V_i} = \frac{H_0 + \frac{H_0}{\omega_0^2} s^2}{1 + \frac{s}{\omega_0 \cdot Q} + \frac{s^2}{\omega_0^2}}$$

s_0 ,


$$a_0 = H_0$$

$$a_2 = H_0 / \omega_0^2$$

for B.P.F, $\Omega = \frac{f_0}{B.W}$

$$\boxed{\Omega = \frac{f_0}{B.W}}$$

$$(B.W)_{3dB}$$

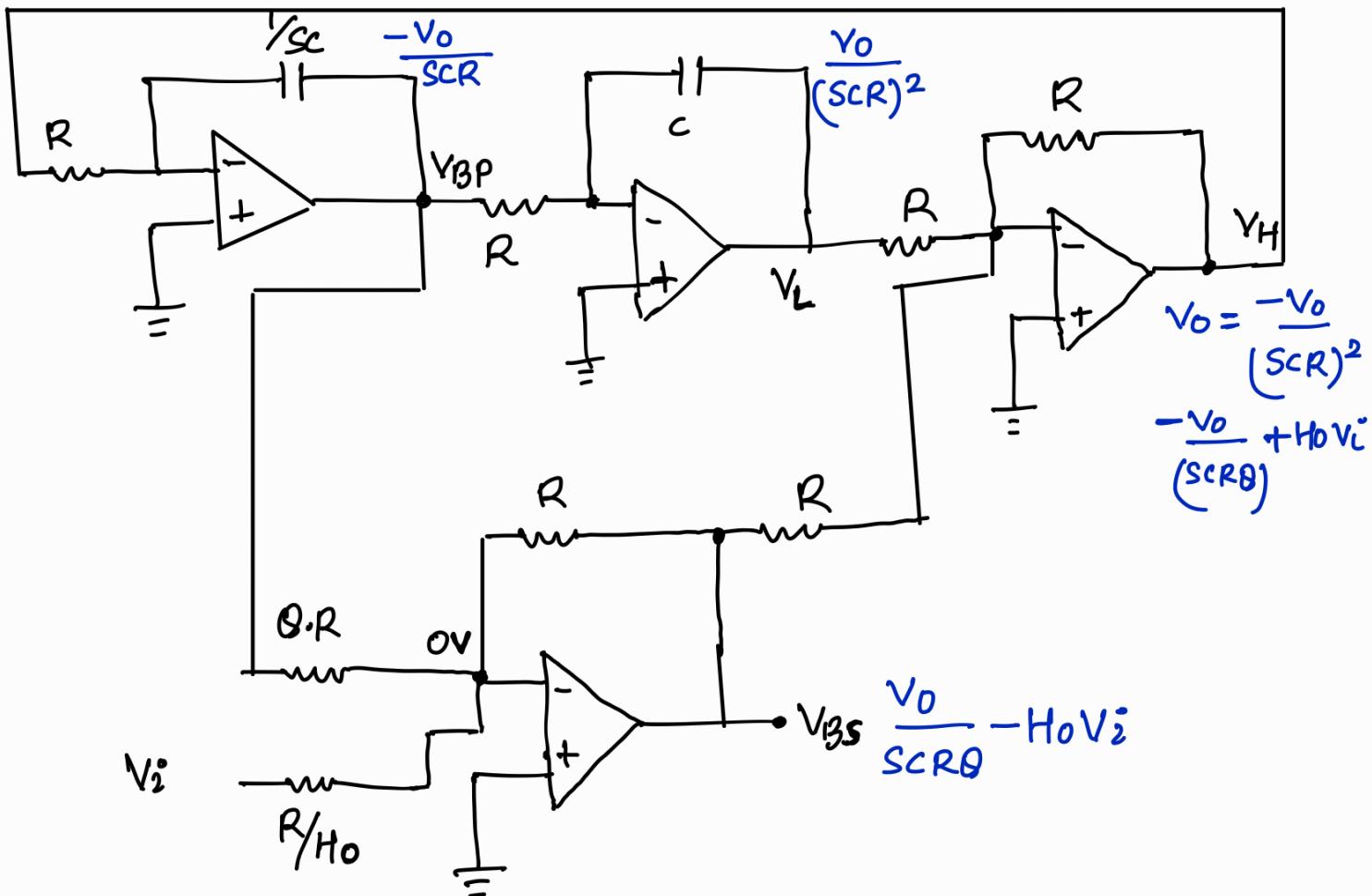

$$V_o = \frac{-V_o}{(SCR)^2} - \frac{V_o}{(SCRQ)} + H_0 V_i$$

$$V_o \left[1 + \frac{1}{(SCR)^2} + \frac{1}{SCRQ} \right] = H_0 V_i$$

$$\frac{V_H}{V_i} = \frac{V_o}{V_i} = \frac{H_0}{1 + \frac{1}{(SCR)^2} + \frac{1}{(SCR\theta)}}$$

$$\frac{V_H}{V_i} = \frac{H_0 (SCR)^2}{\left((SCR)^2 + \frac{SCR}{\theta} + 1 \right)}$$

* High pass filter gets integrated to form Bandpass.

$$\frac{V_{B.P.}}{V_i} = \frac{H_0 (SCR)}{\left((SCR)^2 + \frac{SCR}{\theta} + 1 \right)}$$

* B.P. filter gets integrated to form Low pass.

$$\frac{V_{L.P.}}{V_i} = \frac{H_0}{\left((SCR)^2 + \frac{SCR}{\theta} + 1 \right)}$$

* All pass is combination of B.P., H.P & L.P, such that location of zeroes is mirror image of location of poles.

$$(V_{BSF})_{T.F.} = (V_{L.P.})_{T.F.} + (V_{H.P.})_{T.F.}$$

$$\frac{V_{BS}}{V_i} = \frac{\left[1 + \frac{s^2}{w_0^2} \right] H_0}{\left[1 + \frac{s}{w_0\theta} + \frac{s^2}{w_0^2} \right]},$$

$$w_0 = \frac{1}{RC}$$

θ = Quality factor,

Ability of Universal Active filter

→ To simulate any 2nd order system with poles always on left half plane and zeroes anywhere on 'S' plane.

Calculation for Q

$$\frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$\left| \frac{s}{\omega_0} = \frac{1}{2Q} \pm \sqrt{1 - \frac{1}{4Q^2}} \right| \quad \rightarrow \text{Poles of Universal filter,}$$

for $\boxed{Q \leq \frac{1}{2}}$ } $\left\{ \begin{array}{l} Q = \frac{1}{2} \rightarrow \text{critical damping} \\ (E=1) \end{array} \right. \quad \left. \begin{array}{l} \\ \end{array} \right\}$

Underdamped $\rightarrow E < 1$

Critically damp. $\rightarrow E = 1$

Overdamped $\rightarrow E > 1$

Undamped $\rightarrow E = 0$

$Q < \frac{1}{2} \rightarrow$ exponential, negative real axis.
 $Q > \frac{1}{2} \rightarrow$ Overdamped system

when θ is high \rightarrow Equal to the natural frequency of system.

Ringing freq. =
$$\boxed{\omega = \omega_0 \sqrt{1 - \frac{1}{4Q^2}}}$$
,

\rightarrow No. of rings visible = value of θ .

\rightarrow Phase sensitivity is highest at $\omega = \omega_0 \approx$ Resonance freq.

$$\boxed{\left. \frac{\partial \phi}{\partial \omega} \right|_{\omega=\omega_0} = \frac{2\theta}{\omega_0}}$$

\rightarrow Phase detectors are used for tuning filters.

\rightarrow Higher the ' θ ' \rightarrow sharper the Notch.

\rightarrow Use of notch filter \rightarrow To remove unwanted powerline frequency.

Phase \rightarrow (0 to 2π)


0 to π \rightarrow one pair of poles,

above π \rightarrow occur due to zeroes,

\rightarrow Can be used as spectrum analyzer for periodically zeroed fundamental frequency \rightarrow Picked up at Bandpass filter o/p.

Rest of harmonics occur @ Bandstop O/P.

Integrator

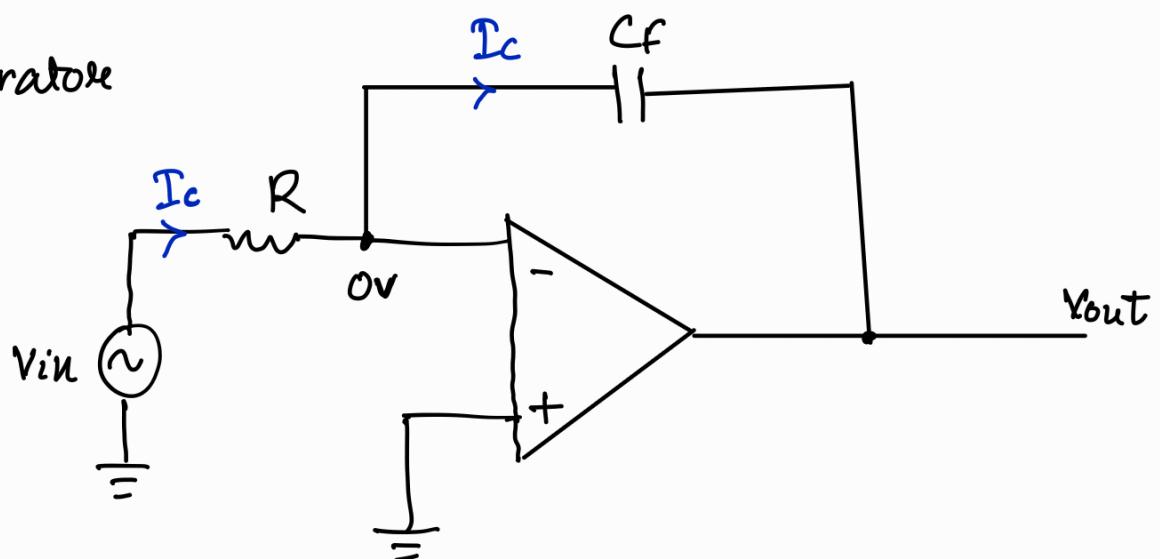

$$\frac{V_{in} - 0}{R} = I_c, \quad I_c = C_F \frac{dV}{dt}, \quad Q = CV$$

Cap \rightarrow not changing with time.

$$\frac{V_{in}}{R} = C_F \cdot \frac{dV_C}{dt} = C_F \times \frac{d}{dt} [0 - V_{out}]$$

$$V_{out} = -\frac{1}{RC_F} \int V_{in}(t) dt + V_{out}(0^+)$$




$$X_C = \frac{1}{\omega_C} = \frac{1}{2\pi f C}, \quad V_{out} = -\frac{X_C}{R} \times V_{in}$$

$$A_V = -\frac{X_C}{R}$$

$$|A_V| = \frac{1}{2\pi R C_f f}$$

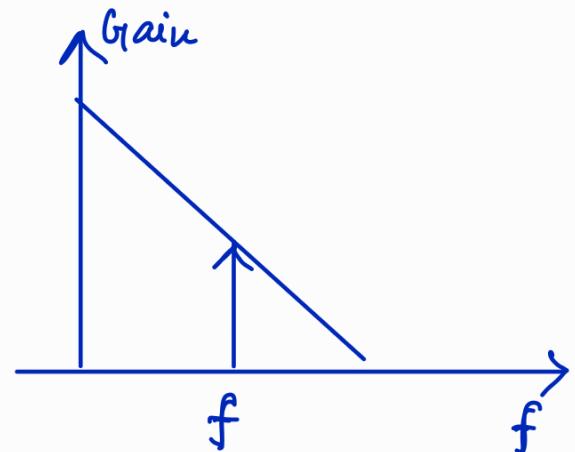
$f \uparrow \rightarrow \text{Gain} \downarrow$.



→ g/p offset voltage of practical opamp.

→ g_u practical → Put feedback resistor II with C_F .
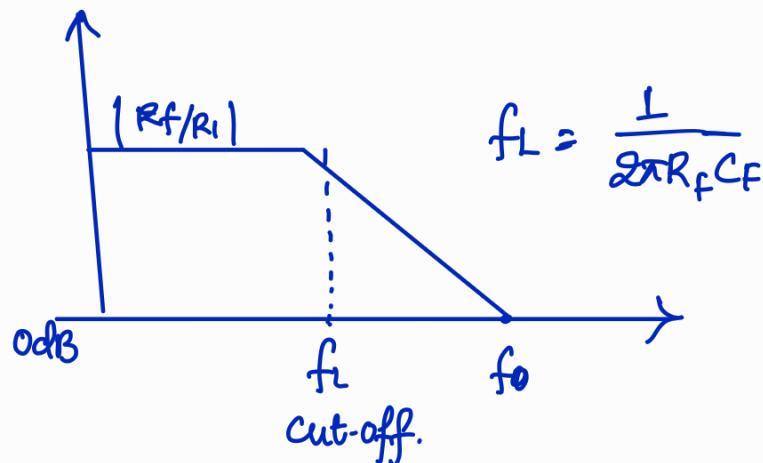
$$\text{So, } A_V = -\frac{R_F}{R_L} \text{ at lower freq.}$$



$$f_L = \frac{1}{2\pi R_f C_F}$$

For proper integralⁿ input freq. (f_s) $> 10f_L$.

2/P freq. should lie b/w $f_L \& f_o$.

Resistor Noise

$$\overline{V_n^2} = 4K_b T_a \cdot R \Delta f$$

absolute temp.

Voltage Bandwidth

Boltzmann's constant
($1.38 \times 10^{-23} \text{ J/K}$)

Resistor Noise spectral density

$$N_0 = \sqrt{(\overline{V_n^2})/\Delta f} = \sqrt{4 K_b T R}$$

Noise due of operational amplifier

$$\overline{V_n^2} = \int_{-\infty}^{\infty} S_{uu}(j\omega) |H(j\omega)|^2 df$$

S_{uu} = Noise spectral density of Noise source,

$$|H(j\omega)|^2 = \frac{1}{(1+2\pi R_f C)^2}$$

$$N_0 = \sqrt{\frac{\overline{V_n^2}}{\Delta f}} = \sqrt{\alpha \frac{kT}{C}}$$

α = order $\rightarrow \alpha \uparrow \rightarrow \text{Noise} \uparrow$.

$$\text{Total Noise} \rightarrow \overline{V_n^2} = \sum_{u=1}^n \int_{-\infty}^{\infty} S_{uu}(j\omega) |H_u(j\omega)|^2 df$$